

THE DAGE INDUSTRIAL TV CAMERA

By **HAROLD E. ENNES**
Staff Eng., Indianapolis Broad., Inc.



Fig. 1. One application for the Dage camera is the unattended monitoring of a machining operation. Picture can be observed on a standard TV receiver.

Its compact size, well-designed circuit, and the fact that it can be used with an unmodified, standard TV receiver has captured industry-wide attention. Here is data on how it is built and how it can be used.

THE inevitable expansion in use of electronic devices in industry is opening another doorway to opportunity. The new field of industrial or general "closed-circuit" television systems is on the verge of vast national enlargement, comparable only to the billions soon to be circulating in TV broadcast transmitters and receivers. The application of electronic "eyes" provides unlimited extension to the arms of industry, science, research, education, and business. A large share of the responsibility for proper servicing and maintenance of such systems will be charged to the independent television service industry.

A recent development in this field is already resulting in the national interest needed to spark large scale activity in closed circuit TV systems. This development is the Dage ITV Camera (manufactured by Dage Electronics Corp., Beech Grove, Indiana) technically described in this article. The low price and relative simplicity of setup and use are factors contributing to an assured broad utilization.

Fig. 1 shows the Dage camera in unattended operation allowing remote observation of functions. In the simplest installation, the a.c. cord is plugged into a 117-volt outlet and a single interconnecting 73-ohm cable is run from the camera output to the antenna terminals of any standard TV receiver. A simple matching transformer is used for 300-ohm input re-


ceivers. The picture from the camera is received on one of the television channels (2 through 6) and is selected and tuned in exactly the same way as a standard broadcast station is tuned. Any number of cameras at different locations can be fed into a single receiver, or a number of receivers at different viewing points can be connected to one or more cameras, as shown in Fig. 2. No modification of any kind is necessary in the receiver, making practical the pur-

chase of inexpensive receivers where desirable.

The camera is a completely self-contained transmission system with only 17 tubes including the Vidicon pickup tube, video amplifiers, sync generator, regulated power supply, kinescope camera monitor, and composite modulated r.f. output. The unit is 9 3/4" high, 4 1/2" wide, 14" in length, and weighs only 18 pounds.

The miniature size of the Dage camera is achieved, in part, by use of

Fig. 2. How a number of cameras at different locations can be fed into a single receiver or how a number of receivers at different viewing points can be connected to one or more cameras. No receiver modifications are required in this TV setup.

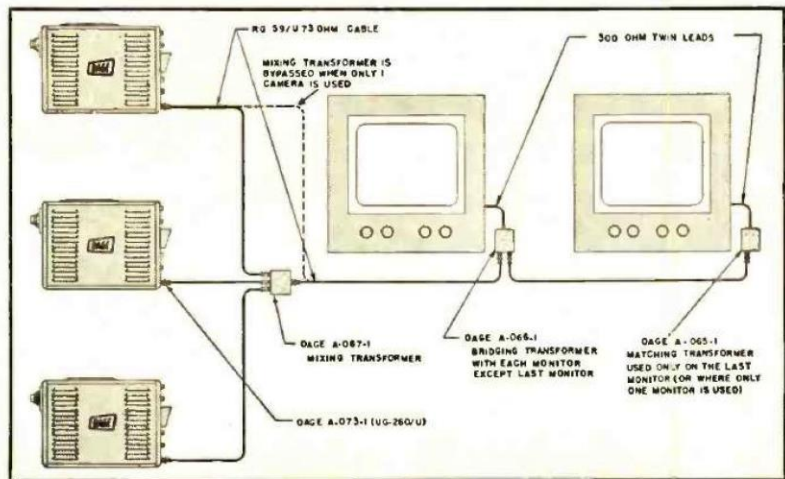

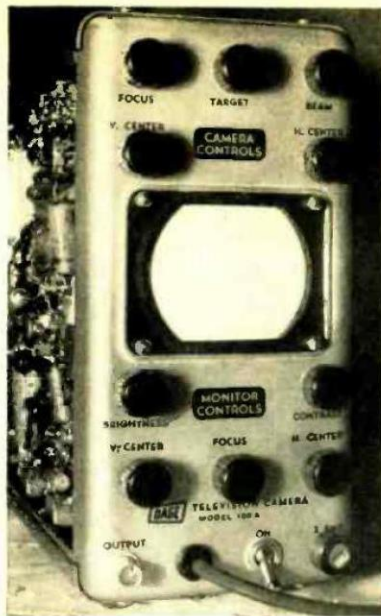


Fig. 3. Rear panel view of the Dage camera showing various camera and monitor controls.

the newly-developed RCA Vidicon pickup tube, type 6198. This pickup tube is only $6\frac{1}{4}$ inches long by 1 inch in diameter. Familiarity with operational characteristics is important to an understanding of camera operation. Since this tube has not been widely publicized in technical details, a very brief review follows of pertinent points. Fig. 4 is an exaggerated "functional" drawing to illustrate basic operation.

The scanning beam is supplied by a conventional electron gun with a 6.3 volt heater used to heat a thermionic cathode placed at ground potential. Four grids are used with the following functions: *Grid #1* (control grid) Picture cut-off value from -45 to -100 volts. *Grid #2* (accelerator grid) Ordinarily operated at a fixed positive voltage in the vicinity of 275 to 300 volts. *Grid #3* (focusing electrode) Current in the external focusing coil

provides a uniform magnetic field through which the scanning beam is swept by the deflection coil saw-tooth currents. *Grid #3* potential between plus 200 and plus 300 volts provides an electrostatic field in conjunction with the magnetic field to focus the electron beam at the photoconductive target. Current through the external focusing coil is fixed in the Dage camera, and grid #3 voltage is made variable to allow optimum electrical focus. *Grid #4* (decelerator electrode) This is a fine mesh screen adjacent to the photoconductive layer and attached to grid #3. This electrode is therefore maintained at the same operating potential as grid 3. The physical configuration provides a uniform field on the beam side of the target so that the beam strikes the photoconductive layer perpendicularly, irrespective of the angle from which approach is made. Decelerating action results from the fact that the signal electrode is operated at a much lower voltage of plus 20 to 30 volts. A low-velocity scanning beam results similar to that in the broadcast type image orthicon; but here the similarity ends.

The light-sensitive element may be visualized as being comprised of two separate elements electrically; (1) a transparent conductive film coating on the inner surface of the glass faceplate, and; (2) a thin layer of photoconductive substance on the scanned side. This is obviously highly exaggerated in the drawing. A metal ring around the front end of the tube serves as the signal lead connection, to which the load resistor is connected in series with the "B plus" supply. The scanning beam is in series with the complete signal circuit. The resistance of the photoconductive layer is dependent upon the amount of light striking it through the lens, being very high under no-light conditions, and less in ratio to the increase in light. One plate of the electrically separate plates is charged to the plus voltage on the signal electrode, while the other plate is charged down to cathode potential by the scanning beam. The remaining beam electrons

are turned back in the form of a return beam under the influence of the positive grids, but is not used in the Vidicon.

Under no-light conditions when the photoconductive element exhibits the characteristics of an insulator, very little current flows through the complete signal path. What little current does flow is termed the "dark current" which is a limiting factor in maximum signal electrode voltage. When light reaches the tube, the transparent conducting film on the inner surface of the glass faceplate begins conduction by an amount dependent upon the light intensity at that particular point, causing the corresponding point on the gun side to rise slightly toward the plus potential of the target supply. Thus the beam current increases at the points of the positive potential pattern created on the gun side of the target in accordance with the light distribution in the focused image. It is noted that the signal current through the load resistor increases for light portions and decreases for dark portions of the image, resulting in a positive black signal at the grid of the first pre-amplifier tube.

The scanning area of the Vidicon is only $\frac{1}{2}$ " wide by $\frac{3}{8}$ " in height. A 3" lens therefore is a "telephoto" type lens for a Vidicon tube, covering a field of 10 by 13.3 feet at a distance of 80 feet. A 1" lens is the general purpose type and a $\frac{1}{2}$ " lens is used for "wide angle" applications.

The spectral response under incandescent lighting is approximately the same as the human eye. Response may also be obtained in the infrared and ultraviolet regions. Only 50 to 100 foot-candles of incident illumination is required with a $\frac{1}{2}$ " or 1" lens (f1.5), and a readable picture can be obtained from the Dage camera with 10 foot-candles of light.

Camera and Monitor Controls


External controls for the camera and built-in monitor are shown in Fig. 3. Fig. 5 shows the interior layout. The monitor uses a 3" kinescope (3RP1) with P1 phosphor. This serves as an excellent "range finder" for lens and camera adjustments where the monitoring receivers may be out of visual range of the camera setup.

The group of "Camera Controls" perform the following functions:

Focus—Varies voltage on grid 3 (focusing grid) of Vidicon. (See block diagram, Fig. 6). In practice the lens focusing collar is adjusted for proper distance to obtain sharp optical focus, then the "Focus" control is adjusted for maximum resolution of picture detail. A resolving power of 350 lines is possible in this camera.

Target—Adjusts voltage on photoconductive target of Vidicon. See Fig. 6. Variation of this control affects the quality of the picture in relation to amount of light on the transmitted scene. For a given operating

Fig. 4. "Functional" diagram which illustrates basic operation of the Vidicon tube.

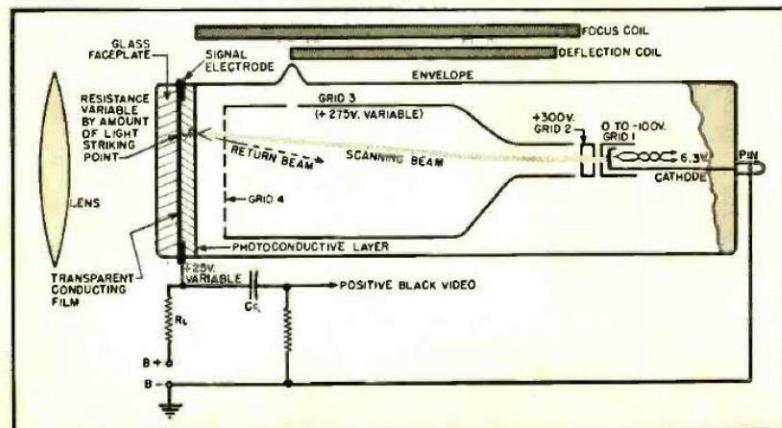

voltage the sensitivity and dark current both tend to gradually change throughout the life of the tube, making mandatory an adjustable voltage to compensate for these changes. Under low light level conditions, the control may be operated toward full clockwise position (maximum voltage) for increased sensitivity. There is, however, a limiting value of target voltage beyond which the non-uniformity of the dark-current background in the picture reaches intolerable proportions. With sufficient light, the picture is improved by reducing the "Target" control setting.

Beam—Adjusts the negative potential of grid 1 (control grid) in the Vidicon. At a fully counterclockwise position (maximum negative voltage) the beam is cut off and no picture appears. As the control is adjusted clockwise, fixing amount of beam current by decreasing negative grid potential, the picture is observed to "wipe clean" with the brightest areas coming in last. The low-lights or dark portions of the scene appear first since the beam is sufficient to resolve the darker (less positive) areas, but insufficient to discharge the brighter portions (more positive) areas. The "Beam" control is left just clockwise of the point where there is enough beam current to resolve all high-lights, since further rotation causes loss of resolution by the well-known spreading of an electron beam with too much beam current.

V. Center—A control in the camera vertical output stage V_{10} which adjusts the magnitude of d.c. in the vertical deflection coil of the Vidicon. This centers the sweep vertically.

H. Center—A control in the camera horizontal output stage V_{12} which adjusts the amount of d.c. in the horizontal deflection coil for the Vidicon. This centers the sweep horizontally.

The camera "Monitor Controls" are self-explanatory with the exception of the "Contrast" control. This control is actually in the cathode of the second video amplifier stage (V_2) and determines the gain of the video amplifier. As such, it affects the contrast of the picture on the viewing receivers as well as the camera monitor. The gain is variable over a range of approximately 10 db. It is often found desirable in practice to set this control about $\frac{1}{4}$ to $\frac{1}{2}$ open, and vary the contrast over a fine range by the "Target" control described previously. The "Contrast" control, however, provides a more flexible adjustment for meeting the requirements of different viewing receivers.

Video Amplifiers

As indicated in Fig. 6, four 6CB6 video amplifier stages are employed. Essentially uniform response to over 4 mc. is achieved by the use of combination series-shunt peaking circuits in all stages except the "high-peaker" stage V_2 . Input stages between the pickup tube and first video amplifier are notably lacking in high-frequency

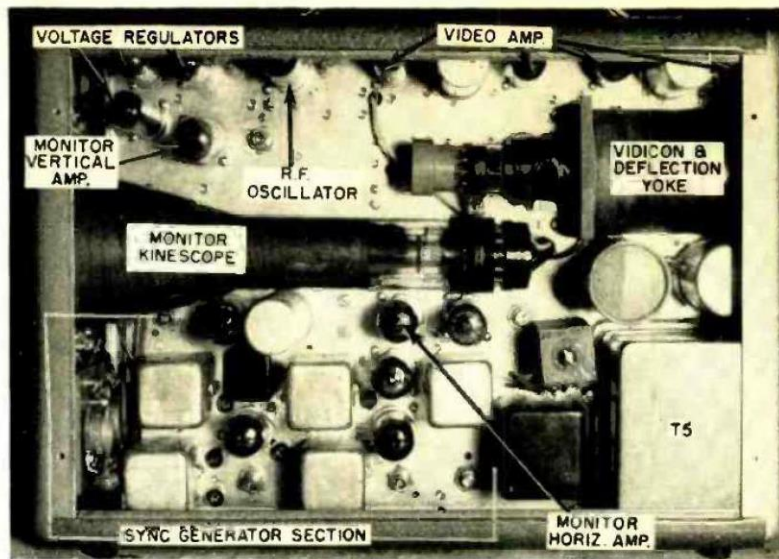


Fig. 5. Internal view of camera showing layout of chassis on the tube side of unit.


response due to the inherently large shunt capacitances of such circuits. It is the purpose of the "high-peaker," V_2 , in the *Dage* camera to compensate for this deficiency by a deliberate boosting of the high-end of the response curve in this stage. This is accomplished by using a very low value of plate load resistor (120 ohms) in series with an inductance. This arrangement provides an essentially inductive load at the higher frequencies in the desired passband, resulting in the necessary high-frequency boost for a flat overall response curve.

The "Contrast" control mentioned before is a 100 ohm variable potentiometer in the cathode of this stage, allowing a 10 db variation of stage

gain. This control may actually be left in the minimum gain position and still provide sufficient contrast in most applications, with judicious setting of "Target" and "Beam" controls.

As noted from Fig. 6, the Vidicon grid #2 (accelerator grid) pin 5, is operated at a fixed plus potential of approximately 275 volts from the low voltage filter supply. The "Focus" control R_3 , resistor R_2 and "Target" control R_1 form a voltage divider from pin 5 to ground. This provides the proper range of voltage adjustments for "Focus" and "Target" electrodes. The signal current variations through coupling resistor R_4 provide the signal voltage for the following first video amplifier stage through coupling con-

Fig. 6. Block diagram of the camera. An RCA type 6198 Vidicon pickup tube is employed.

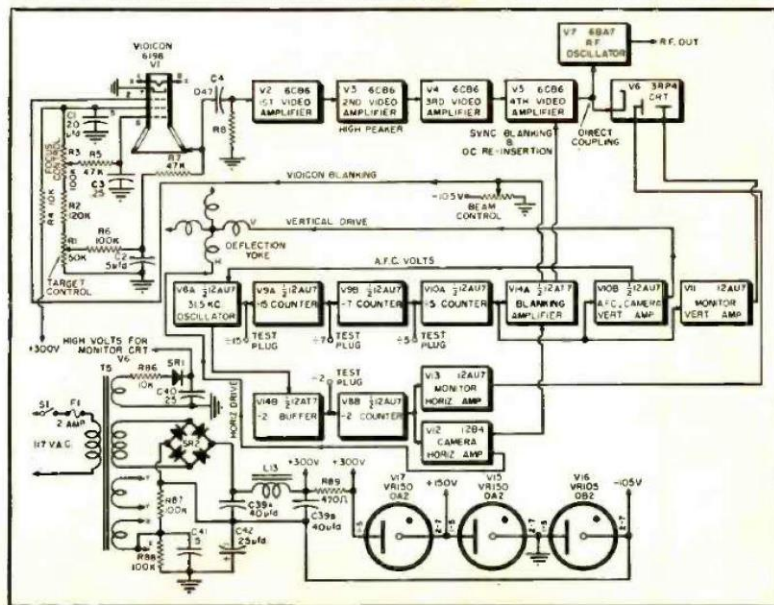

STAN-BURN E-PARKE

CATHODE RAY TUBE SPECIALS
One Year Guarantee

C. E.		STAN-BURN	
*STP4	\$44.95	*10BP4	\$11.00
*7JP4	17.10	*12LP4A	14.20
*10BP4A	19.25	*14CP4	17.00
*10FP4A	24.00	*15DP4	19.50
*12KP4A	27.10	*16AP4	21.60
*12LP4A	21.70	*16FP4	19.60
*12UP4B	28.25	*16GP4	21.60
*14CP4	24.50	*16EP4	22.60
*16AP4A	30.95	*16DP/HP4	19.60
*16BP4A	28.20	*16DP/HP4A	20.60
*16GP4	31.25	*16KP4	18.50
*16HP4/16RP4	28.20	*16LP4	21.60
*17BP4A	23.90	*16LP4A	20.60
*17CP4	23.90	*16LP4A	18.50
*19AP4A	39.45	*17CP4	21.60
*20CP4	24.75	*19AP4	23.90
*20LP4	37.50	*19AP4A	25.90
*21EP4A	37.35	*20CP4	29.50
*24AP4A	78.50	*21EP4	32.50

ANTENNAE SPECIALS

*REG DOUBLE 1/2" Antenna	1.11	12 or more
*RMS EVA 100 DOUBLE 1/2" Antenna	\$2.29	\$2.09
*Antenna	2.49	2.39
*10 Element Coils	3.55	2.55
*Folded H; Straight Low Quick Rig	4.25	3.25
*15 Elements	4.05	3.75
*WINDOW CONICALS	1.60	1.40
*5 FOOT SWEGGED MASTS	.79	.69
*10 FOOT PLAIN	1.39	1.29
*NEPCO MASTS	1.60	1.40
*42 Mil. TV WIRE	\$ 9.95 M FL.	
*55 Mil. 300 OHM	11.95 M FL.	
*72 OHM COAXIAL	38.00 M FL.	
*12" Heavy Slug Speaker	Special \$3.98	

CHASSIS 630 REGAL with Cascade Tuner \$149.50
OPEN FACE CABINET 42.00

WIRE RECORDERS IN STOCK
Model 973C - 2-speed Tape Recorder - Write for Price.
RADIO CRAFTSMAN
Model C400 - Hi-Fi Amplifier Net 42.90
Model C100 - AM-PM Tuner Net 131.50
Model C500 - Williamson Amplifier Net 99.50
We also carry MASCO-ROGEM-PILOT, etc. Amplifiers, Pre-Amps, FM Tuners and WEBSTER Tape Recorders.

649 PM Speaker - 5 3/8" 630 Vert. output
7" PM Speaker - 3.98 630 Vert. output
7711 G.E. Flyback 1.98 630 Vert. Blocking
70" Yoke 1.98 OSC. Xform. .89
630 Vert. output Cascade Tuners 19.95
upright 1.98 Dumont 21.25 mc. 14.95

AUTHORIZED DISTRIBUTORS for General Electric, Kenrad, Tung-Sol, National Union, De Wald, Regal, Automatic and General Motors.
Automatic Custom-Built Radios for Plymouth, Ford, Chevrolet and many others, always in stock.
We carry a Complete line of HI-FIDELITY and sound equipment. Send us your requests.
We also carry a complete line of popular makes of Radio Tubes at 50% discount. Also many other special purpose and transmitting tubes, and all electronic parts and equipment at lowest prices. Send us a list of your requirements for prompt quotations.
Terms: 20% with order, Balance C.O.D. All prices F.O.B. NEW YORK Warehouse. Minimum order \$5.00.
Write for our latest price list and Hi-Fi catalog to Dept. RN-7.

STAN-BURN RADIO and ELECTRONICS CO.

(C.E.S. THEATRE BLDG.)
1497 BROADWAY • NEW YORK 19, N.Y.

Please Mention
RADIO & TELEVISION NEWS
When Answering Advertisements

110V. AC POWER SUPPLY FOR ANY 274-N RECEIVER

Just plug it into the rear of your 274-N RECEIVER... any model. Complete kit and black metal case, with ALL parts and diagrams. Simple and easy to build in a jiffy. Delivers 24 volts plus B voltage. No wiring changes to be made. Designed especially for the 274-N receiver. Only \$8.95.
Filament trans. for 274N receivers. Pri. 110V, 60 cy. AC. Sec. 24V @ .6A. An excellent buy at \$1.95 ea.

SPLINED TUNING KNOB FOR 274N RECEIVERS

An exclusive O.K. item manufactured for us. Fits BC-959, BC-154 and other 274N receivers. This is a really hard-to-obtain item. Only .89c ea.

OFFENBACH-REIMUS
1564 Market Street, San Francisco, Calif.

Dage TV Camera

(Continued from page 34)

the high-side of an audio oscillator adjusted to 15,750 cps. In this way the audio oscillator beats with the second harmonic provided by the 31,500 cycle master oscillator and a zero beat may be obtained from the use of the germanium diode. Listening to the phones, the operator varies the 31,500 cycle "Adjust" control (screwdriver-adjust chassis control) in the grid circuit of the master oscillator for zero beat. Although a number of tones may be heard, depending upon how far out of range the 15,750 cycle "Adjust" control in the -2 circuit happens to be, variation of the master oscillator control allows the operator to distinguish the second harmonic beat from the others. After this zero beat is obtained, the 15,750 cycle "Adjust" control is varied for zero beat with the remaining tone. An oscilloscope connected to "Test Plug +2" will now show the pattern illustrated in Fig. 7. This indicates that every second pulse is syncing the +2 counter whose free-running frequency is close to 15,750 cycles.

Germanium diodes are employed in the interstage coupling networks of each vertical divider chain to bring the firing time into synchronism and for effective stage isolation to prevent interaction. Each divider is accurately adjusted by connecting the oscilloscope to the "Test Plugs" for that particular divider as noted in Fig. 6. Fig. 11 shows the pattern obtained at "Test Plug +15" indicating that every 15th pulse synchronizes the oscillator when the 2100-cycle "Adjust" control (31,500 ÷ 15) is properly adjusted. The same procedure is carried out through the remaining ÷7 and ÷5 counters. Tube V_{15A} is the final countdown for the vertical pulses, supplying 60 pps to the blanking amplifier V_{15B} , the camera vertical pulse amplifier V_{15C} and monitor vertical amplifier V_{15D} .

The blanking amplifier V_{15A} receives the vertical pulses on the grid, while

Fig. 11. "Divided by 15" counter pulses on scope when connected to "Test Plug +15". Every 15th pulse triggers ÷15 oscillator.



4 for 53 NEW

Trav-Electric CONVERTERS

CHANGE 6 OR 12 VOLT D.C. TO 110 VOLT A.C. 60 CYCLE
Just plug into Cigar Lighter on Dash.



Trav-Electric Super
Model 6-71160
60 cycle
60-75 Watts
\$37.95 LIST

Size 4"x5"x6" Operates
• Wire Recorders • Dictating Machines
• Amplifiers • Turntables
• Soldering Iron • Small Electric Drill



Trav-Electric Master
Model 6-51160
60 cycle
40-50 Watts
\$24.95 LIST

Size 4"x5"x6" Operates
• Curling Irons • Small Dictating Machines
• Radios • Test Equipment, etc.
• Turntables • Portable Phonographs



Trav-Electric Senior
Model 6-11160
60 cycle
35-40 Watts
\$15.95 LIST

Size 2 1/2"x2 1/2"x4 1/2" Operates
• Test Equipment • Short, Long Wave Radios
• Turntables • Portable Phonographs
• Lights • Electric Shavers, etc.



Trav-Electric Midget
Model 6-11160
60 cycle
10-15 Watts
\$10.95 LIST

Size 2"x2"x3 1/2" Operates Test Equipment, All Electric Shavers

Fully Guaranteed
See Your Jobber or Dealer
TERADO COMPANY
MFGS. OF PRECISION EQUIPMENT
1068 RAYMOND AVE. • ST. PAUL 14, MINN.
In Canada write: Atlas Radio Corp., Ltd.
560 King St. West, Toronto 28, Ont.
Export Sales Division: Scheel International, Inc.,
4237 N. Lincoln Ave., Chicago 18, Ill., U. S. A.
Cable Address—Harscheel

SELECTED SURPLUS

NON-INDUCTIVE RESISTORS **59¢**
Ohmite, 250 Ohm, 100 Watt. Special, 5 for \$2.50

SOLA CONSTANT VOLT. TRANSF.
Pri. 95-125 volts, 60 cy. Sec. Regulated. \$ 9.95
at 115 volts. 30 VA. 120 VA. \$22.50

OIL CONDENSER SALE

2 MFD-2500 VDC	\$2.95	3.75 mfd 660VAC	\$2.45
4 MFD-2500 VDC	5.95	1 mfd 7500VDC	1.75
7 MFD-3000 VDC	3.95	1 12KV DC	2.95
1 MFD-4000 VDC	5.95	.01x .01 12KV DC	2.95
1 MFD-5000 VDC	2.95	5 mfd 660 VAC	2.95

6 HY, 400 MA FILTER CHOKE
Made by Acme. Only 30 Ohms DC Res. **\$2.50**
ALL BRAND NEW.
Priced at a fraction of cost. 3 for \$6.50

0-150 MICROAMP METER
G.E., 2" Bush Bakelite case. Scale 0-150 Microamps. BRAND NEW. A Terrific Value. **\$4.95**

G.E. PLATE TRANSFORMER
Pri. 120 V., 60 cy. Sec. 1140 Volts Ct. @ 1 amp. Ideal for Bridge Rect. Fully Cased, Herm. Sealed. In original cartons. ONLY...ea. **\$16.95**

MOBILE DYNAMOTORS

MADE BY PIONEER AND EICOR

6 Volts Input. 425 Volts at 375 MA Output. 6 1/2" Long. 4" Diameter. Weight 10 lbs. List Price Approx. \$70.00. **\$24.95**
BRAND NEW, ONLY

CARTER SUPER DYNAMOTOR

12 Volts Input. 400 V. Output @ 200 MA Continuous or 375 MA Intermittent duty. Model B420. Designed for Police, Aircraft and Marine Use. Small, rugged and efficient. **\$24.95**
BRAND NEW, ONLY

G. E. RELAY CONTROL

(Ideal for Model Controls, Etc.)
Contains a sigma midget 8,000 ohm. relay (trips at less than 2 MA), high impedance choke, bimetal strip, neon pilot and many useful parts. The sensitive relay alone is worth much more than the total low price of **\$1.25** Each 10 for **\$9.90**

PANEL METERS
NEW GOV'T SURPLUS STANDARD BRANDS

METER BUY OF THE YEAR!

2" METERS

0-10 MA AC	\$2.95
0-50 Microamps	\$8.95
0-100 Microamps	7.95
0-200 Microamps	6.95
0-500 Microamps	5.95
0-100 Milliamps	4.50
0-150 Milliamps	4.50
0-200 Milliamps	4.50
0-300 Milliamps	4.50
0-500 Milliamps	4.50
0-1000 Milliamps	4.50
0-50 Volt DC	4.95
0-150 V. DC (1 MA)	4.95
0-1.5 Volts AC	4.95
0-3 Volts AC	4.95
0-150 Volts AC	7.50
0-15 KV DC multiplier	0.95

4" METERS

0-200 Microamps	\$8.95
-----------------	--------

WIRE WOUND RESISTORS
Stock too long to list. We can supply most sizes, so order what you need.

5 Watts. From 1 Ohm to 40K Ohms. Ea. \$.09
10 Watts. From 1 Ohm to 70K Ohms. Ea. .15
25 Watts. From 1 Ohm to 30K Ohms. Ea. .20
25 Watts. From 1 Ohm to 100K Ohms. Ea. .30
50 Watts. From 5 Ohms to 100K Ohms. Ea. .40
100 Watts. From 50 Ohms to 100K Ohms. Ea. .50

ADJUSTABLE SLIDER, WIRE WOUND

10 Watts from 1 Ohm to 10K.	\$.25
25 Watts from 20 Ohms to 2.5K.	.35

VACUUM CONDENSERS

50 mmf. 32 KV, Eimac.	\$9.95
50 mmf. 20 KV, Jennings.	7.95

1 MEGOHM, 1% W.W. PRECISION RESISTORS, SHALLCROSS, ONLY 97¢ ea. 10 for \$8.95

BAKELITE CASED MICAS

NFD VDC	Price	NFD VDC	Price	NFD VDC	Price
.001 500	\$.24	.01 1 KV	\$.45	.02 2 KV	\$.90
.002 600	.24	.02 1200	.35	.005 2500	.55
.01 600	.28	.02 1500	.65	.002 2500	.45
.02 600	.26	.03 1500	.75	.004 2500	.50

Min. Order \$3.00-25% with Order

PEAK ELECTRONICS CO.

66 West Broadway, New York 7, N. Y.
Phone WO 4-5439

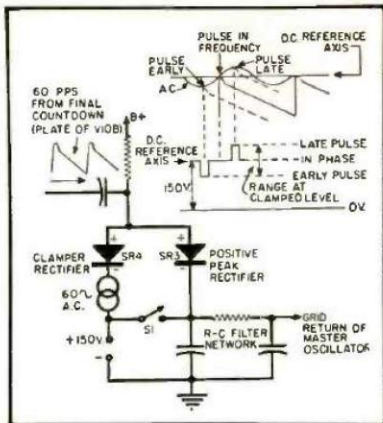


Fig. 12. The clamping-comparison line lock.

horizontal pulses are injected on its cathode from the V_{12} stage. In this manner the composite sync-blanking pulses of negative polarity appear at the plate and are injected into the grid of V_3 as described for Fig. 8. Fig. 9 shows the rectified composite output signal displayed at line frequency, and Fig. 10 illustrates the field frequency.

Horizontal and vertical size and linearity controls for Vidicon sweep are incorporated as screwdriver-adjustable chassis controls. The amplitude of vertical sweep ("Camera Height Control") is determined by the setting of a potentiometer in the grid excitation branch of V_{10B} . A separate potentiometer across the resistors which determine the bias on the V_{10B} grid serves to adjust the tube transfer-curve characteristics and is the sweep "Vertical Linearity Control". The two adjustments are obviously interdependent in action. The camera "Width Control" is an adjustable condenser between the ± 2 counter output (V_{5B}) and the camera horizontal output stage V_{12} .

The master oscillator can be locked in operation by the 60 cycle a.c. power line frequency by means of a unique clamping-comparison circuit. Two selenium diode rectifiers are used as indicated in the simplified schematic of Fig. 12. The action is based upon the fact that the blocking time of the oscillator is dependent not only upon the RC time constant of its grid circuit, but also upon a static grid potential which determines the extent to which the grid condenser may charge during the "on" time. Pulses from the final vertical countdown (60 pps) are combined with a fixed d.c. potential upon which is superimposed a 60 cycle a.c. line voltage, and the resultant clamped voltage is used to vary this static grid potential and automatically correct the master oscillator frequency.

The fixed reference d.c. potential is applied at the cathode of SR_1 in series with the a.c. filament winding Y-Y (Fig. 6). The anodes of SR_2 and SR_3 are parallel connected across a d.c. potential and pulses from the

SUMMER CLEARANCE PRICES SLASHED

T.V. TUBES—ROCK BOTTOM PRICES

In lots of 6 each No. only

6866	89c	6C66	39c	6A05	38c
19606	89c	6AK5	89c	6C06	51.05
12AX7	47c	6D06	57c	654	49c

Tube Special—Broken Keys—Electrically Perfect
12A6...29c 4 for \$1.00 12A8...49c 7 for \$3.00
Tube Sale—2A7-55-27-83-31-56...6 of Any Type \$2.25

Heavy Duty Shielded P.P. Input Trans. \$1.00
H.D. Silver Contact Trans. Keys. 1.00
Bat Handle S.P.S.T. or D.P.S.T. Toggle Switch. 25c

Isolambi Octal Panel Clamp Sockets. 3c ea.
100 Assorted Resistors. \$1.95
1 mfd., 1,000V Oil Filled Cond. 75c
2 Gang Var. Cond. 45K K.C. with Osc. Section.
2 1/2" In. Pulley on 3/4" Shaft. 49c

Westinghouse Kuprox Rectifier 0.64 Amp. 25
Volts. Reg. \$11.00 ea. Special. \$1.95

BRAND NEW 10" PHONO RECORDS—Ass't.
Jazz—Popular. Rhythmic—Blues. Please specify.
12 for \$1.79 or 24 for \$3.00

Slide Pole—10 Pos. 2 Gang Switch. 29c
Grind your own Crystals. Pure Brazilian Quartz. Vari-
ous sizes and thicknesses. 5/16 lb. pkg. \$1.00
4 Tube Drilled Chassis. 4 1/2" x 8 1/2" x 1 1/2". 29c each
Signal Corps Phones—2 M. Ohms (8 M. Ohms
Imp.) \$1.25
2 Ft. Ext. Cord (incl. Plug). 40c

TOBE TUBULAR ELECTROLYTICS

20-20 MFD. 150 V. .49c	30-30 MFD. 150 V. .57c
40-40 MFD. 150 V. .59c	

Low-Loss Short Wave
Lock Type Air Trimmer
Variable Condensers
5 Pl.—20Mmfd. 14c
7 Pl.—25-30 Mmfd. 15c
8 Pl.—30-35 Mmfd. 16c
14 Pl.—56 Mmfd. 24c

3 GANG T.R.F.
VARIABLE CON-
DENSERS
D 2 N 3 C R 8
000385 Con. 65c

D.P.D.T. SLIDE
TOGGLE
SWITCH 15c

1,000 OHM WIRE WOUND POTENTIOMETER 15c
10 MV. FILTER CHOKE SHIELDED 3 for \$1.00

PIEZO CRYSTAL HOLDERS. 12 for \$1.00—\$6.00 per C

RCR Band Switches—
3 Gang, 3 pos. 3 band. 30c 4 gang, 4 pos. 4.5 band. 40c
Trimmer-Padder Ass't. all insulating. \$2.25
Wires—100 Ass't. 25c

ATTENTION: Prospector, Explorer or Hidden Treasure? Construct a U.S. Army Type of Metallic Mine Detector Amplifier. Amplifier unit only (less tubes and batteries with cables, headphones and jack). Army wiring diagram. Type AN/TRS-1. \$2.95
Phileo push button Rotary Switch Double Pole. 35c
8 or 9 Gang Push Button Switch. 40c

DRILLED CHASSIS FOR 5-6 tubes 5" x 10" x 1 1/2". 25c
PHONO JACKS—DIPES & CLEARIN ADJ. 18c
156-1 RATIO VERNIER DIALS—In. 3/8 in. Hub. 35c
SALE—PHONO (RECORD) ALBUMS—12—3 comp.—15c
10"—1 comp.—25c; 1 comp.—20c; 12 comp.—60c

VULCAN HEAVY DUTY 100 WATT SOLDERING IRON.
Built for U.S.N.—Brand New—Early sells for
\$8.50 OUR PRICE \$2.99

MINIMUM ORDER \$3.00—NO C.O.D.
SHIPMENTS—PLEASE INCLUDE POSTAGE
NEWARK SURPLUS MATERIALS CO.
324 Plane Street, Dept. JY, NEWARK 1, N. J.

SAY YOU SAW IT IN RADIO & TELEVISION NEWS

COMPLETE TV AERIAL KIT

Consisting of:

- H.L.W. antenna
- 7 ft. heavy duty mast
- 75 ft. 300 ohm wire
- 50 ft. guywire
- Sturdy swivel base
- 6 stand-off insulators

Special **475** Boxed
Priced

STRAIGHT LOW TV AERIAL AR27

Only **175**

Service man's array. Pre-assembled. Lo-band array only, with mast clamps for mast up to 1 1/2".

10% CASH WITH ORDERS

VALMO RADIO CO.

509 ARCH ST. & 6205 MARKET ST.
Philadelphia, Pa.

6th & ORANGE STS. • Wilmington, Del.
4401 VENTNOR AVE. • Atlantic City, N. J.
1133 HADDON AVE. • Camden, N. J.
317 Park Heights Avenue • Salisbury, Md.

final countdown (hence dependent upon master oscillator frequency) are injected at this point. With the "Line-Lock" switch S, closed (unlocked position) the static grid potential is fixed by the d.c. potential of 150 volts. The comparison function is shorted out in this position of the switch. With S, open (line-lock position) the cathode of SR, is varied above and below the d.c. reference potential at the 60 cps line rate. Injection of the 60 pps from the final countdown to the anodes results in a clamped value at SR, dependent upon the relative frequency with the 60 cycle variation. SR serves as the positive peak rectifier for the clamped pulse. If the master oscillator and all frequency dividers are exactly adjusted, the 60 pps coincide with the 60 cycle variations, and the voltage is clamped at the d.c. reference potential. (See waveforms, Fig. 12.) If the 60 pps from the final counter are early or late (too high or too low in frequency) the clamped level falls in the negative direction or rises in the positive direction. The level change is filtered to pure d.c. correction at the output of the filter network to which the master oscillator grid is returned. The direction of change is such that the cut-off period is shortened if the frequency was too low, or lengthened if the frequency was too high.

The author wishes to thank George Fathauer, inventor of this system and president of the *Dage Electronics Corp.*, for supplying the technical data on the camera and permission to publish this article.

-30-

WIRELESS OPS OF "OLD"

FOR some time we have been considering a column dedicated to "Old Time Wireless Operators"—not "Radio Operators" for that appellation is too modern. We believe that we may have something along that line in the near future as our mail has brought us a reminder that 1952 was the 40th anniversary of the sinking of the "S.S. Titanic" in the North Atlantic and the subsequent employment of a large number of wireless operators for our American passenger ships.

It was in 1912 that our radio men put on long pants and became an integral part of American shipping. What has become of these men? Through this column we are going to try and find out what goes with the "Old Timers."

Our compliments to all "Old Timers" of 1912 and thereafter and we would certainly appreciate your writing us as to when and where you first became a "commercial" operator, either ashore or afloat and by whom you were employed. We would also like to know how long you continued as a commercial radio operator and what you are doing now. A recent picture of yourself would also add interest to the column as would career highlights.

We feel that your story will be of interest to our readers, so you old brass pounders get busy and write us, in care of this column, and watch for its early appearance.

-30-

July, 1953

SEE LEO FIRST FOR . . .

hallicrafters

I can SAVE you money... Liberal Trade-ins



LEO I. MEYERSON
WØGFO

JUST ARRIVED! THE NEW 100 WATT HT-20 XMTR—\$449.50



\$179.50

S-76 RECEIVER

Extra selectivity with double superhetro-dyne circuit. One RF, two conversion and 3 IF stages. Range 550-1550 Kc, 1.7-34 Mc in four bands. 8 tubes plus voltage regulator and rectifier. Complete with tubes, less speaker.



\$224.50

SX-71 RECEIVER

Double Conversion sharp selectivity, plus built-in NBFM at moderate cost. 11 tubes plus voltage regulator and rectifier. Low down payment.

NAME YOUR TERMS • LOW DOWN PAYMENTS • PERSONALIZED SERVICE

HALLICRAFTERS RECEIVERS AVAILABLE FOR IMMEDIATE SHIPMENT

S-81	\$49.50	S-40B	\$119.95	ST-83	\$129.95
S-82	\$49.50	S-53A	\$ 89.95	S-78A	\$ 89.50
A-84	\$99.50	S-72L	\$119.95	SX-62	\$299.50
S-38C	\$49.50	S-77A	\$119.95	S-72 Portable	\$109.95
R-46 Speaker			\$19.95	SX-73	\$975.00

Famous WRL RADIO REFERENCE MAP 25c



CU on 10-20 & 75 Meters

NEW LOG BOOK 25c

For mobile or fixed station. Spiral binding. Full columns and listing all FCC required info. Will accommodate 1,525 stations. "Q" signals, phonetic alphabet, amateur international prefixes.

PHONE 7795

WRITE—WIRE



IT'S NEW! IT'S FREE!

WRL 1953 CATALOG

Send for your copy today. Contains everything new in radio and television. Jam-packed with bargains. Leo I. Meyerson, WØGFO



Send For FREE Copy

WORLD RADIO LABORATORIES

744 West Broadway

Council Bluffs, Iowa

R-7

Please send me:

Radio Map 25c

SX-71 Info

New Catalog

S-76 Info

Used Equipment List

New Log Book 25c

Name

Address

City

State

SPEAKER RECONING

Complete line Cones, Spiders, Rings and Voice Coils. Custom Built Voice Coils. Low prices. Write for Parts List and Reconing Information.

WESTERN ELECTRONICS CO.

3164 West Colfax Denver 4, Colo.

ON-THE-SPOT BATTERY RECORDER

WALKIE-RECORDALL 8 lb. miniature BATTERY RECORDER-PLAYBACK Continuous, permanent, accurate. Indexed recording at only 3c per hr. Instantaneous, permanent playback. Picks up sound up to 60 ft. Records conferences, lectures, dictation, 2-way phone & sales talks, while walking, riding or dining. Records in closed television with "hidden mike"! Write for Detailed Literature.

MILES REPRODUCER CO., INC.

812 BROADWAY Dept. TR-7, NEW YORK 3, N. Y.

GET INTO ELECTRONICS



You can enter this uncrowded, interesting field. Defense expansion, new developments demand trained specialists. Study all phases radio & electronics theory and practice: TV, FM, broadcasting, satellite aviation, marine, police radio. 18-month course. Graduates in demand by major companies, U.S. or equivalent required. Begin Jan. March, June, Sept. Campus life. Write for catalog.

VALPARAISO TECHNICAL INSTITUTE
Dept. RD Valparaiso, Indiana